

High-power (≥50W) Brick package DC/DC Converters Application Guide2022

I. Selection Guide.....	3
A. Confirm Power Supply Specifications.....	3
B. Power Distribution System Design.....	4
II. DC/DC Converter Testing Suggestions.....	7
A. Test Circuits and Methods.....	7
B. Basic Electrical Performance Tests.....	8
a) Output voltage accuracy:.....	8
b) Line regulation:.....	8
c) Load regulation:.....	9
d) Cross adjustment rate.....	10
e) Efficiency:.....	10
f) Ripple and noise:.....	11
g) Dynamic load:.....	12
h) Start-up time:.....	13
i) Isolation and insulation:.....	14
j) Temperature rise test:.....	15
k) Heat treatment evaluation of DC/DC converter.....	15
l) Input Reflection Ripple Current Test:.....	16
III. Applications of DC/DC Converters.....	16
A. Input and Output Filtering Circuit.....	16
B. Electromagnetic Interference and Electromagnetic Compatibility.....	18
C. Capacitive Load.....	19
D. Pin-out.....	20
a) TRIM.....	20
b) Remote on/off control (sense).....	20

c) Switch control.....	21
IV. FAQs.....	22
A. Do MORNSUN's DC/DC converters support hot-plug?.....	22
B. Can MORNSUN's DC/DC converters be used at no-load or light-load?.....	22
C. Reasons cause start-up failures of MORNSUN's DC/DC converters?.....	23
D. Operating temperature.....	24
E. Measures to suppress noise.....	24
F. Over-temperature protection.....	24
G. Thermal Design Recommendations.....	24

I. Selection Guide

A. Confirm Power Supply Specifications

The first step is to confirm specifications of the power supply and then determine to choose a standard power supply or a customized one according to requested parameters.

Step 1, select the input voltage range

Select appropriate nominal input voltage and its corresponding input voltage range according to the actual application. For applications that the supply voltage does not change much, such as the communication industry -48V bus input and industrial DC bus input, a product series with narrow range (2:1) input can be selected, such as VR(C) series with nominal 48V input and voltage input range of 36-75V; For applications that the input voltage changes greatly or that are compatible with multiple voltage inputs, such as battery power supply in the railway industry, all kinds batteries (lithium batteries, dry batteries, storage battery, etc.) and long-distance transmission, it is recommended to choose wide range input series, such as UR series (4:1) or UWR(T) series (12:1).

Step 2, select the output voltage

Common output voltages are 3.3V、5V、9V、12V、15V、24V、28V、48V、54V,etc.

Step 3, select the output power

Output current can be determined once the load is confirmed. The load current determines power and affects the converter's reliability and price. It's suggest to use the converter in 30%-80% of its power at ambient temperature. In high temperature or low temperature environment, derating should be taken into account. Choosing a right output current is one of the key factors in successful design. Inappropriate current will lead to lower reliability and high cost.

In the case of high temperature and poor heat dissipation condition, the module with larger size or bigger package is preferred when with the same power. For the application that works in a high-temperature environment for a long time, it is necessary to do heat treatment, such as air cooling or heat sink and shell for heat-dissipating, to avoid triggering the product over-temperature protection and causing the system to work abnormally.

Step 4, select the isolation

The isolation feature makes the input and output of the module to be two separate power supplies (non-common ground). In industrial bus system, Isolation helps rise the loop's resistance

in harsh environments (lighting, arc interference) and isolates noise in analog circuit and digital circuit in hybrid circuit and converts voltages in multiple voltage power system. For converters with dual or multiple outputs, it is necessary to confirm whether the outputs need to be isolated. If isolation is required, products offering dual or multiple isolated outputs would be the choice.

Step 5, select the package

It needs to take dimension, cost and the converter's reliability into account. Enough space should be reserved for the converter to reduce the interference to signal acquisition as its thermal radiation and the interference to other circuit components.

In short, it's best to select a standard package as far as possible, to meet lower cost, mature technology, less challenge of development and save development time.

For converters that have special requirements for high isolation, wide voltage range input, high temperature, EMC, UL certification and others, please contact our sales for more information.

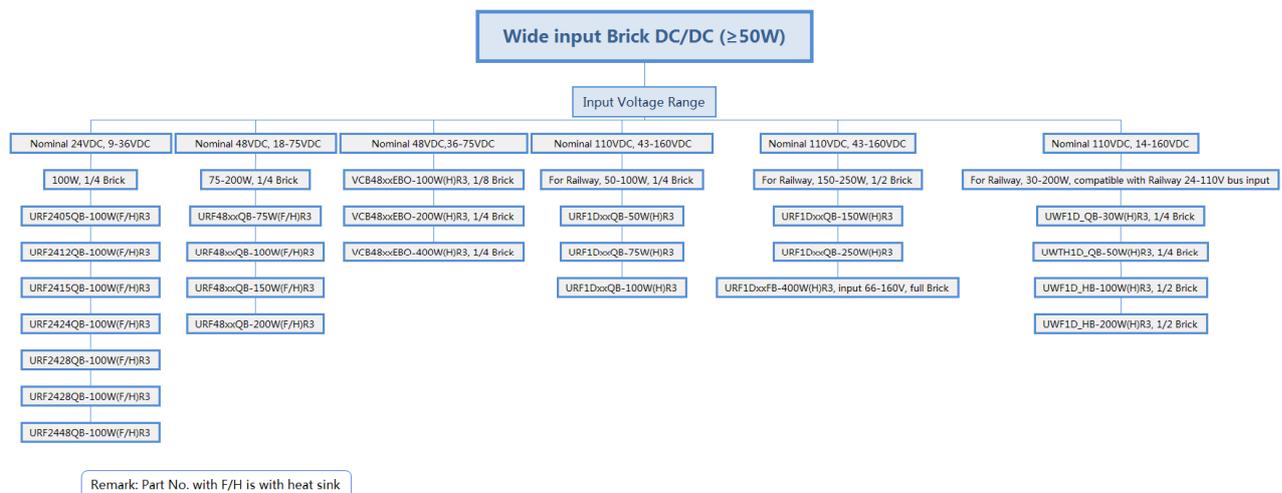


Diagram 1-1 Selection Block Diagram

B. Power Distribution System Design

Products' features and circuit's requirements should be taken into consideration when engineers design a power distribution system. And they have to optimize the system several times, by which acquires accurate operating parameters and environmental parameters of practical circuits to precisely choose suitable converters.

Step 1, ambient factors

Ambient factors include ambient temperature, transmission distance and so on.

Ambient temperature can affect converters and external components. Considering that the converters are used in high temperature, low temperature or high and low temperature cycle (such as: engine room and cabin), corresponding parameters may change. Engineers should clearly know these changes and design correct circuit in this application. It should be noted that the working ambient temperature of power module refers to the internal temperature of the device rather than the device case or ambient temperature. Generally, the former is very different from the latter in that the device contains many heat-generating components.

Industries	Working temperature
Commercial	0-70°C
Industrial	-40-85°C
Vehicle on-board equipment	-40-105°C
Field exploration instrument	-55-85°C
Military	-55-125°C

Table 1-1 Working temperature of different Industries

It also should be noted that the module derates significantly at high temperature. Under high temperature, the chosen converter should allow significant deration and connect an electrolytic capacitor with excellent high and low temperature performance. Please refer to datasheet when selecting the capacitor.

In an environment where there is interference such as arc, electrostatic discharge, unstable AC power grid, starter switch, relay, lightning strike, etc., the input voltage and current may far exceed the tolerance of the module, resulting in permanent damage to the module and paralysis of the load circuit. At this time, it is necessary to add a protection circuit to ensure the safe operation of the power supply.

Transmission distance is another factor affecting converters and external components. General suggestions are:

- a) Wide input and isolated, high-efficiency converters are the best choices for long-distance transmission. In addition to lightning protection, accurate transmission loss should be calculated.
- b) If the transmission distance is long and the loss is large, the power supply of the module must provide enough power to ensure the normal operation of the module. Considering the start-up current of the module, it is generally recommended that the current provided to the power supply is 1.4-1.6 times the input current of the module at low-voltage input, which should be combined with the load condition, line loss, and other peripheral losses.
- c) It is recommended to connect a capacitor at the input terminal of the converter to improve start-up performance itself.

Step 2, working circumstance.

A common sense is that all converters lose certain power and change it into their own heat energy, which will make surrounding environment warmer. Further, it causes data interference (heat-sensitive components) and performance degradation of devices. Thus, larger ventilation or heat dissipation space to reduce temperature rise is essential to ensure stability and reliability of the system.

As DC/DC converters adopt switching technology, their own switching oscillator circuit and internal magnetic components will produce electromagnetic interference and pollution to surrounding ones by conduction and radiation. EMI cannot be completely eliminated, but can be reduced to a safe level by certain measures for electromagnetic compatibility.

Step 3, layout.

Unreasonable grounding and layout easily tend to cause unstable system, high noise and other undesirable phenomena.

In many applications, analog circuit and digital circuit share the same power supply, in which it is very important to separately use them or completely isolate the power supply from ground loop. It aims to avoiding the interference from digital DC voltage drop variation and logic suppressor process to analog circuit system.

In high-speed/dynamic analog circuit or digital circuit, the distributed resistance and equivalent inductance become noticeable and easily cause noise interference due to the rapid changes of load current when the load is far away from distribution. In this case, load decoupling and eliminating series impedance of the wire and resonances caused by distribution parameters are recommended.

When multiple heating devices are used at the same time, the distance between the modules should be considered to form a smooth airflow channel, so that the airflow and the heating devices can fully exchange heat. It is recommended that the distance between the heating devices at least meets the following Diagram 1-2.

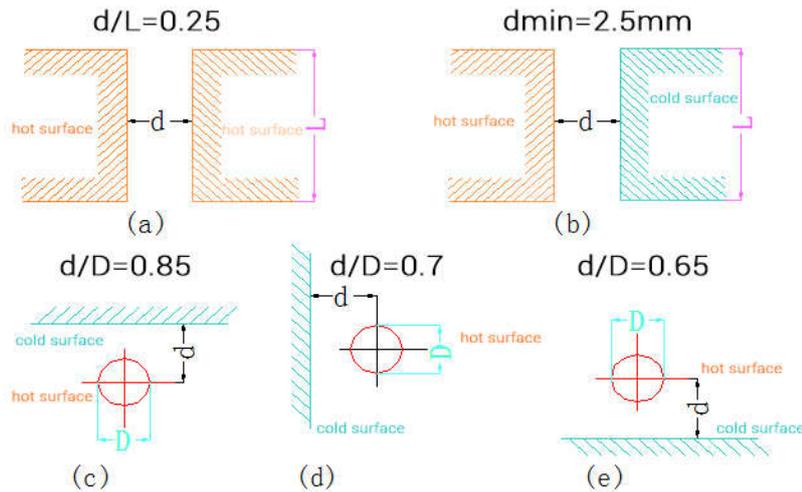


Diagram 1-2 the distance between the devices

II. DC/DC Converter Testing Suggestions

Product's performance in practical application is also vital except a right power supply. Therefore, it needs to be tested and verified before use. Common test methods are available as follows:

A. Test Circuits and Methods

Kelvin test method is a standard one as shown in diagram 2-1. Test conditions: ambient temperature $T_a=25^{\circ}\text{C}$, humidity $<75\%$.

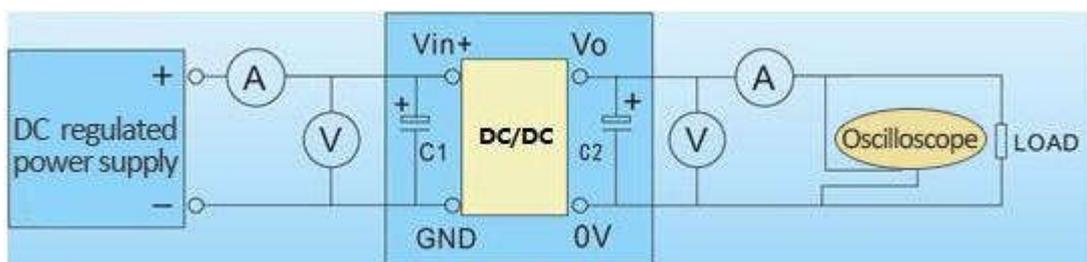


Diagram 2-1 Kelvin test method

Test instruments: DC adjustable regulated power supply (wide enough input voltage range),

ammeter A (accuracy: 0.001A), voltmeter V (accuracy: 0.001V), load resistance

(rated load: $\frac{V_o^2}{P}$, light load: $\frac{V_o^2}{10\%*P}$)

Notes:

- a) Wire connection: the less wire loss, the better it is. A multi-strand copper wire with 1mm diameter is the best choice to avoid excessive voltage drop. When the load current is large, it should shorten distances between output pins and the load, and increase cross-sectional area of the connecting wire to reduce the excessive voltage drop.
- b) When testing ripple and noise, it is suggested to test output by using contact measuring method with a single pole to avoid measurement errors generated by input and output common ground and external interference. (See “ripple and noise”)
- c) For more details please refer to datasheet.

B. Basic Electrical Performance Tests

Performance testing begins with correct connections of power modules, by which to confirm whether parameters meet requirements or not.

a) Output voltage accuracy:

V_{outnom} : output voltage at nominal input voltage and full load	Output voltage accuracy $= \frac{V_{out} - V_{outnom}}{V_{outnom}} \times 100\%$
V_{out} : tested output voltage at nominal input voltage	

e.g. (VCB4812SBO-100WR3): $V_{outnom}=12V$, rated load= 1.44Ω , $V_{out}=12.039V$,

$$\text{Output voltage accuracy} = \frac{12.039 - 12.000}{12.000} \times 100\% = 0.325\%$$

b) Line regulation:

Wide input, regulated output series:

V_{outnom} : output voltage at nominal input voltage and rated load	Line regulation $= \frac{V_{mdev} - V_{outnom}}{V_{outnom}} \times 100\%$
V_{outh} : output voltage at rated load when input voltage at its upper limit	
V_{outl} : output voltage at rated load when input voltage at its lower limit	
V_{mdev} : V_{outh} or V_{outl} which is deviated from V_{outn} more	

e. g. (VCB4812SBO-100WR3): rated load=8.333A, $V_{outh}=5.01V$, $V_{outl}=5.00V$, $V_{outnom}=5.01V$,

$$\text{Line regulation} = \frac{5.00 - 5.01}{5.01} \times 100\% = -0.2\%$$

c) Load regulation:

Wide input, regulated output series:

V_{b1} : output voltage at nominal input voltage and 10% load	Load regulation $= \frac{V_b - V_{b0}}{V_{b0}} \times 100\%$
V_{b2} : output voltage at nominal input voltage and 100% load	
V_{b0} : output voltage at nominal input voltage and 50% load	
V_b : V_{b1} or V_{b2} which is deviated from V_{b0} more	

d) Cross adjustment rate

DC/DC converters offering dual-output or more usually take voltage from the output terminal of primary circuit to form a closed-loop control loop. The primary circuit's load current changes is not significant to its output voltage. However, auxiliary circuit's voltage is obtained through transformer coupling. Both the primary circuit's load current changes and the auxiliary circuit's will lead to great changes of the auxiliary circuit's output voltage. Therefore, the load of each output of these DC/DC converters should be balanced (difference should not more than 5%). Otherwise, the output voltage and load regulation rate will be beyond the accuracy range.

$V_{1(50\%)}$: output voltage at 50% primary circuit's load	Cross adjustment rate
$V_{2(50\%)}$: output voltage at 50% auxiliary circuit's load	
$V_{2(10\%)}$: output voltage at 100% auxiliary circuit's load and 10% auxiliary circuit's load	$= \frac{V_2' - V_{2(50\%)}}{V_{2(50\%)}} \times 100\%$
$V_{2(100\%)}$: output voltage at 10% auxiliary circuit's load and 100% auxiliary circuit's load	
$V_{2(50\%)}, V_{2(10\%)}, V_{2(100\%)}$: output voltage at same circuit	
V_2' : $V_{2(10\%)}$ or $V_{2(100\%)}$ which is deviated from $V_{2(50\%)}$ more	

e) Efficiency:

V_{in} : nominal input voltage	Efficiency
I_{out} : output current at full load	
V_{out} : output voltage at full load	
I_{in} : input current	
	$\eta = \frac{I_{out} \times V_{out}}{I_{in} \times V_{in}} \times 100\%$

e.g. (VCB4812SBO-100WR3): $V_{in}=48V$, $V_{out}=11.951V$, $I_{out}=8.333A$, $I_{in}=2.264A$,

$$\eta = \frac{8.333 \times 11.951}{2.264 \times 48.000} \times 100\% = 91.64\%$$

f) Ripple and noise:

Ripple and noise is the periodic and random AC variation superimposed on DC output, which affects output accuracy and usually is calculated with peak-to-peak (mVP-P).

First, set oscilloscope bandwidth 20MHz to effectively prevent high-frequency noise.

Second, test with parallel cable measuring method, twisted-pair cable measuring method or contact measuring method.

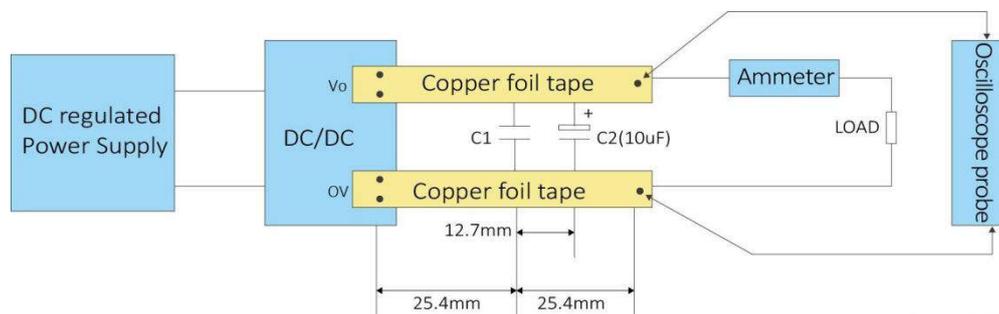


Diagram 2-2 Parallel cable measuring method

Notes:

- 1) C1: a high-frequency ceramic capacitor with 1uF capacitance.
- 2) C2: an electrolytic capacitor with 10uF capacitance and twice withstand voltage higher than that of converters, suitable for wide input products (series prefixed with VR, WR, PW and UR).
- 3) Distance between two paralleled copper foils is 2.5 mm and, of which the sum of voltage drops should be less than 2% of nominal output voltage.

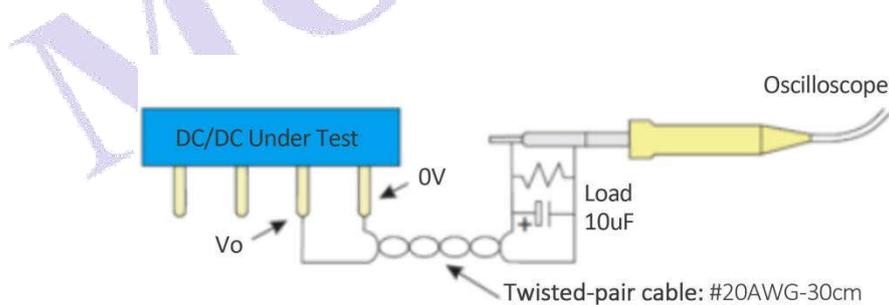


Diagram 2-3 Twisted-pair cable measuring method

Another testing is with twisted-pair cable measuring method as shown above in diagram 2-3.

Connect tested power supply Vo and 0V with a twisted-pair cable which is composed of 30cm long and #20AWG, and then connect a dummy load between them. Next, connect a 10 μ F electrolytic capacitor at the end of the twisted-pair cable, which connects the end of oscilloscope's probe at one terminal and connects the ground at the other.

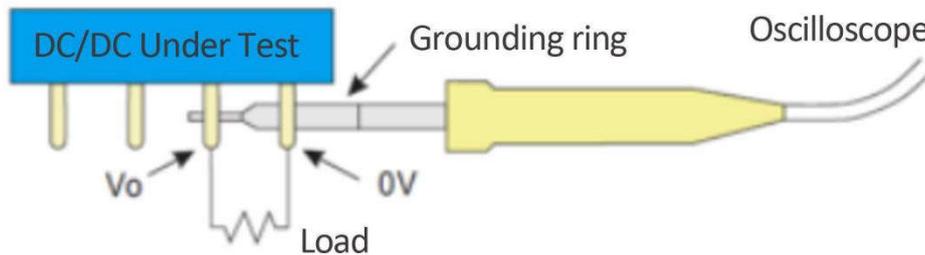


Diagram 2-4 Contact measuring method with oscilloscope

Contact measuring method, as shown in diagram 2-4, is usually adopted for oscilloscope to shield interference. Because the oscilloscope's ground clip could absorb various high-frequency noise, affecting test results. Whatever single output or double outputs or more, the test method is similar. Connect oscilloscope probe to each output terminal. Then actual tested ripple and noise will vary depending on different circuit and external components. Diagram 2-5 shows the actual tested ripple and noise waveform.

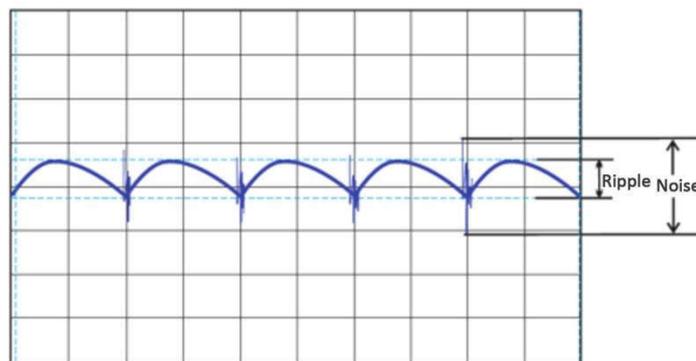


Diagram 2-5 Waveform of Ripple & Noise Test

g) Dynamic load:

When the load varies greatly, all the power supplies have a corresponding response time. During this time, the power supply's output voltage will produce instantaneous overshoot and then return to normal state. Dynamic response is an important indicator of power's performance and is measured by the overshoot and the response time.

The specific measurement method is to use an electronic load to carry out the power load's sudden change. Set the load current at 25% -50% -25% and 50% -75% -50% of the rated load. Next, set current's jumping and falling slope 0.08-0.1A/us. Last, measure the maximum deviation of the output voltage and response time with an oscilloscope. Waveform of dynamic load test is as shown in Diagram 2-6.

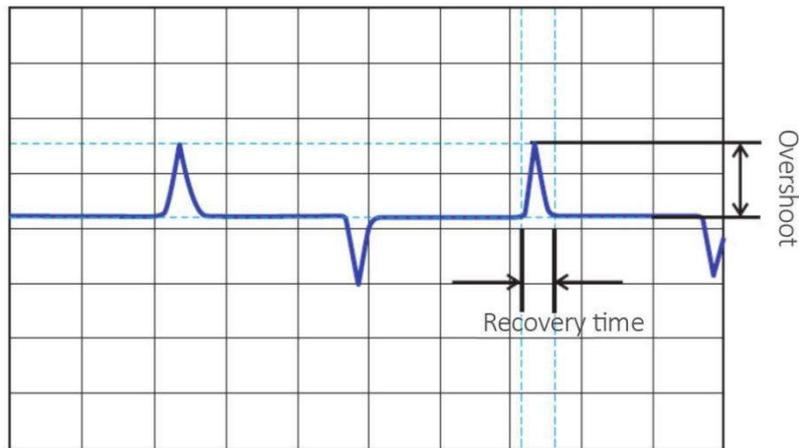


Diagram 2-6 Waveform of dynamic load Test

h) Start-up time:

Start-up time refers to corresponding delay time during which input voltage exists and output voltage reaches to a targeted value, which is also called the delay time. It is found that external filters (including input and output capacitors) can significantly delay the start-up time when tested at rated full load, so in practical design, taking start-up time and ripple and noise into consideration together is recommended. For more details please refer to datasheet or contact our sales department. Diagram 2-7 shows the actual tested start-up time waveform.

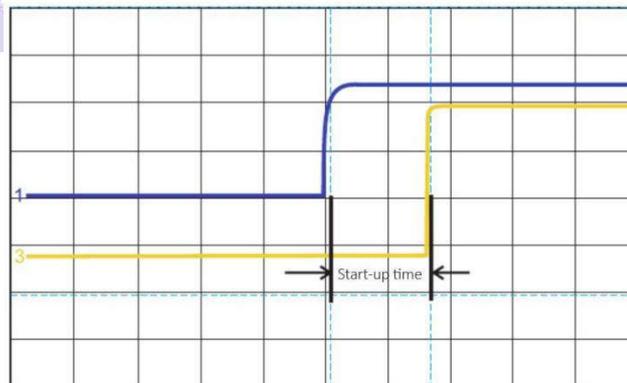


Diagram 2-7 Waveform of Start-up Time Test

i) Isolation and insulation:

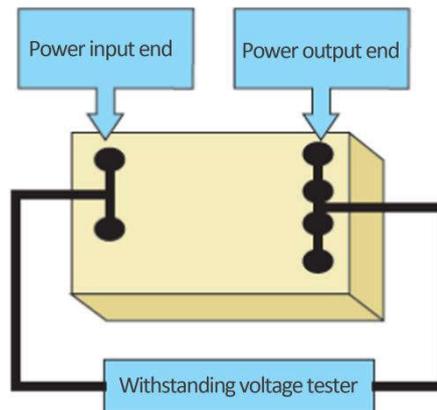


Diagram 2-8 Method of Withstand Test

Withstand test: Following withstand test standards, withstand value shall be set from 0 slowly upward and remain 1 minute at the maximum rated isolation.

Insulation test: measure it for 1 minute by applying isolation voltage between the input and output

Insulation resistance: the value should be above 1GOhm when applying 500VDC between input and output

Isolation voltage shown in datasheet is only valid for a one-minute quick test. Therefore, rated working voltage must refer to relevant standard if it's required longer operation at high withstand voltage. And the switching relationship between the isolation voltage and the rated working voltage, according to the IEC950 standard, is shown as Diagram 2-9. Standard typical breakdown voltage of IEC950 is shown in Table 2-10.

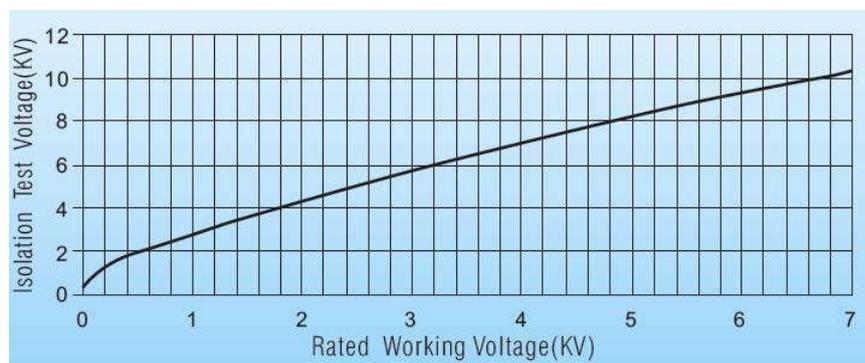


Diagram 2-9 Relationship between Isolation Test Voltage and Rated Working Voltage

Isolation Test Voltage (Vrms)	Rated Working Voltage (Vrms)
1000	130
1500	230
3000	1100
6000	3050

Table 2-10 Typical Breakdown Voltage Ratings According to IEC950

j) Temperature rise test:

Temperature rise test is usually with the help of thermal imager or thermocouple. The former can be affected and lead to a certain deviation in measurement results due to the emissivity. Therefore, the latter, test with thermocouple, is recommended.

For example, given that the ambient temperature T_a is $25\text{ }^\circ\text{C}$, and the measured temperature of power supply T_c is $60\text{ }^\circ\text{C}$. Then the temperature rise ΔT is $35\text{ }^\circ\text{C}$ ($\Delta T = T_c - T_a = 60\text{ }^\circ\text{C} - 25\text{ }^\circ\text{C} = 35\text{ }^\circ\text{C}$).

Test condition: power supply is in nominal voltage input and at rated power.

Note: Temperature of power supply varies due to different power, material of case and internal design, etc. Under the same condition, a metal case has better heat dissipation, lower temperature of internal component and higher reliability than a plastic one. It's recommended, in a closed environment, to keep power supply away from components that are sensitive to temperature or isolate them for no natural ventilation.

k) Heat treatment evaluation of DC/DC converter

When high-power products are used in different situations, there will be different ways of heat dissipation, including forced air cooling, water cooling, external heat sink and so on. According to different actual conditions, the reference value of temperature derating curve in the power module specification will be affected. In this case, open-frame products provide customers with a more convenient heat treatment evaluation - thermal test points. With the help of the thermal test points provided, a targeted evaluation can be made to determine whether the heat treatment made by the system for the power module is sufficient to ensure the stable and reliable operation of the system.

5. Thermal test point

The thermal element is installed on the top surface of the product and dissipates heat to the surrounding environment by conduction, convection and radiation. Sufficient heat dissipation conditions should be provided to ensure the reliable operation of the product. Whether the heat dissipation conditions are satisfied can be verified by the temperature of the thermal test point ① in Figure 5.



Figure 5

Note:

The temperature of the thermal test point ① cannot exceed 130° C, otherwise, the product would not work normally due to trigger over-temperature protection.

Diagram 2-10 example of thermal test point

I) Input Reflection Ripple Current Test:

The input reflection ripple current mainly refers to the periodic and random AC variation superimposed on DC output which is reflected by the converter. It needs an inductor and capacitor elements connected at its front-end to match the source impedance, as shown in Diagram 2-11. Inductance capacitance recommended values: L_{in} (4.7 μ H), C_{in} (220 μ F, ESR <1.0 Ω at 100 KHz).

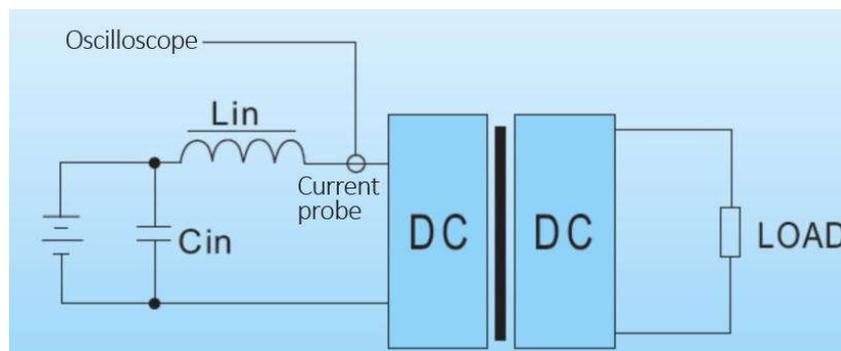


Diagram 2-11 Input Reflection Ripple Current Test

III. Applications of DC/DC Converters

A. Input and Output Filtering Circuit

Filters are usually connected at the input and output terminals of the converters to reduce ripple and noise in applications where are sensitive.

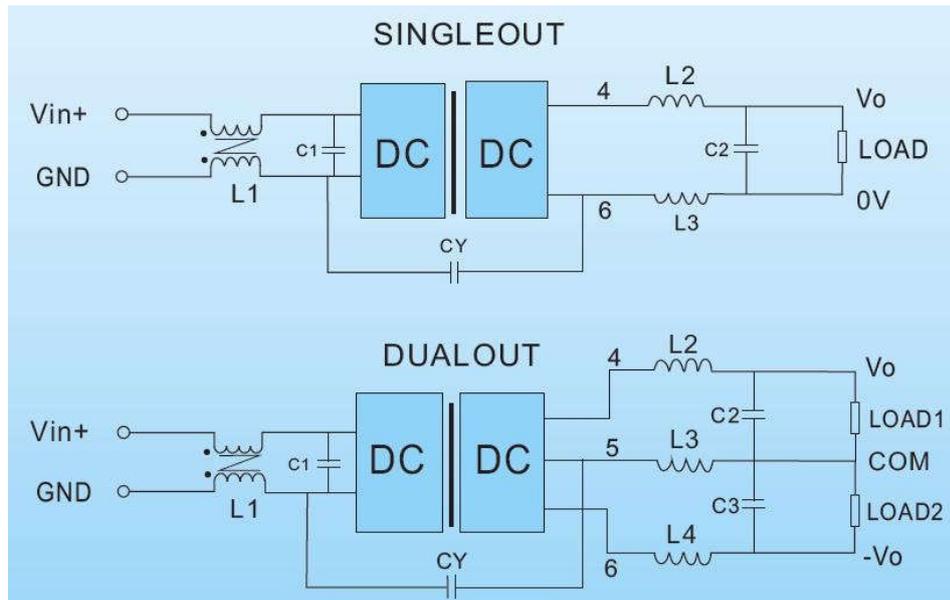


Diagram 3-1 Recommended circuit reducing ripple & noise

Adding a capacitor at the input terminal can absorb the voltage spikes, save the energy and keep the voltage stable. Adding a capacitor at the output terminal can greatly reduce the output ripple, but it's likely to cause the failure of start-up due to too large capacitance or too low ESR. For applications requiring extremely low ripple, using a "LC" filter network or using converters with low ripple is an alternative.

C1: electrolytic capacitors, to reduce input ripple. Its value please refer to datasheet;

L2/L3/L4, C2/C3: forming an LC filter network to reduce the output ripple. The capacitor is suggested to a ceramic capacitor or an electrolytic capacitor with low resistance, whose value is determined according to the actual ripple but cannot exceed the maximum capacitive load;

L1, CY: L1 is a common mode inductor to suppress common mode interference. Y1 is a Y capacitor offering 100-1000pF.

Note:

For the components of the filter circuit, they are generally calculated according to the following formula and the frequency should be one tenth of the converter's switching frequency.

$$f_c = \frac{1}{2\pi\sqrt{LC}}$$

The calculated value of filter may vary due to different application designs and load conditions, so the value must be adjusted in conjunction with the practical application.

When setting the value of the filter capacitor, it cannot exceed the maximum one of the capacitive load indicated in datasheet.

B. Electromagnetic Interference and Electromagnetic Compatibility

a) Electromagnetic Interference (EMI)

Electromagnetic interference (EMI) is a disruption that affects an electrical circuit because of either electromagnetic induction or electromagnetic radiation. It cannot be completely eliminated, but can be reduced to a safe level. Certain effective ways to suppress EMI are generally as follows:

- i) to shield EMI radiation: to select the products in metal shielded package or to add additional shield so as to reduce EMI radiation;
- ii) Reasonable grounding;
- ii) to select suitable filters or filter networks to reduce the transmission of EMI from the wire and the signal line;
- iv) to separately layout the converters and the small signal circuit, in order to effectively avoid the interference of the former to the latter.

b) Electromagnetic Compatibility (EMC)

EMC is the ability of electronic equipment and power supply to work stably and reliably in a certain electromagnetic interference environment. It is also the ability of electronic equipment and power supply to limit their own electromagnetic interference and avoid interference to other electronic equipment.

Improving EMC is available from the following three aspects:

- i) to reduce the radiation of source of EMC interference;
- ii) to shield EMC interference transmission;
- iii) to improve anti-electromagnetic interference of the electronic equipment and power supply.

According to the way of transmission, EMC interference is divided into:

- i) Conduction interference.** It is the noise generated by the system into the DC input line or signal line. The frequency range is 150KHz-30MHz. Conduction interference has common mode and differential mode. LC network is often used to suppress the conducted interference.
- ii) Radiation interference.** It directly spreads in electromagnetic waves, plays a role of launch antenna and its frequency range is 30MHz-1GHz. Radiation interference can be suppressed by metal shielding.

c) EMC Solution-recommended Circuit

As DC / DC converters are secondary power supplies, in order to pass EMS test, they usually connect external protection circuit at the DC/DC port or signal port, and add an inductance between TVS and varistor to discharge most of the interference energy. It can combine the TVS's lower clamping voltage and the varistor's larger flow, protecting the back-circuit. Here's the formula to calculate the inductance's value, where $I_{pp} / 2$ mainly taking a 50% derating of the TVS into account:

$$L = \frac{(Uc1 - Uc2) \times (20 - 8)}{I_{pp} / 2}$$

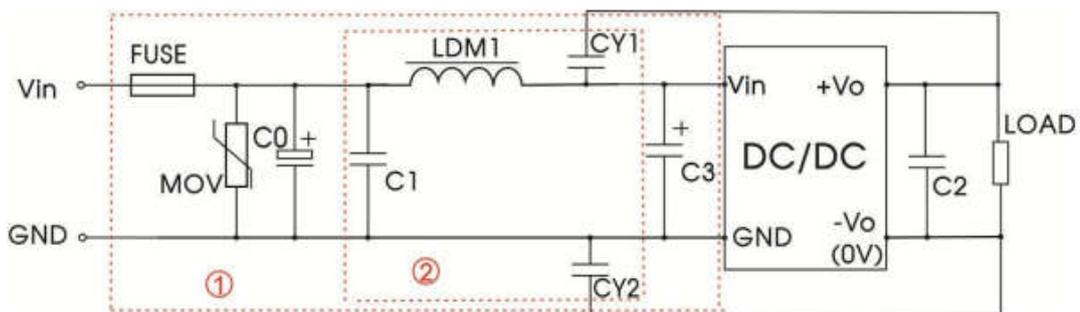


Diagram 3-2 EMC Solution-recommended Circuit

The circuit marked ① is used for EMS to test peripheral circuit. The circuit marked ② is used for EMI filtering and can be selected according to requirements. For more details please refer to datasheet.

C. Capacitive Load

Electrolytic capacitors can be added to the output of the power converter, but general switching

power converter has a maximum capacitive load requirement as too large capacitance or low ESR (equivalent series resistance) may cause the module to work unstable or bad start-up. For more details please refer to datasheet.

D. Pin-out

a) TRIM

The output voltage $\pm 10\%$ around its rated value can be adjusted by adding a resistor at the TRIM terminal. But the total output power of the converter should be within its maximum output power. If the output voltage is higher than its nominal value, lower output current to comply with the maximum output power. If the output voltage is lower than its nominal value, the output current should not exceed the rated current, too.

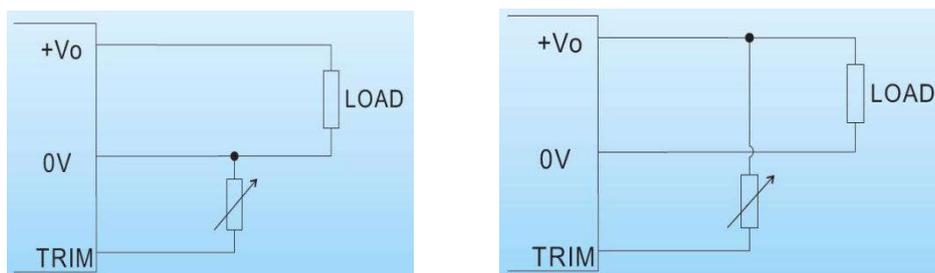


Diagram 3-3 Connection of output voltage's trimming with an external resistor

External resistor connection method is shown in the above diagram. To adjust to a higher output voltage (see left diagram), connecting a resistor between TRIM terminal and output terminal is recommended. To adjust to a lower output voltage (see right diagram), connecting a resistor between TRIM terminal and Vo is recommended. If TRIM is not needed, just no connection.

It also should be noted that the adjustment is a certain range (generally about $\pm 10\%$) and cannot get all required voltages through TRIM. If the required voltage exceeds the range, it may be incompatible to the converter's output over-voltage protection, affecting the normal operation of the converter. In this case, it should take required voltage through other methods.

b) Remote on/off control (sense)

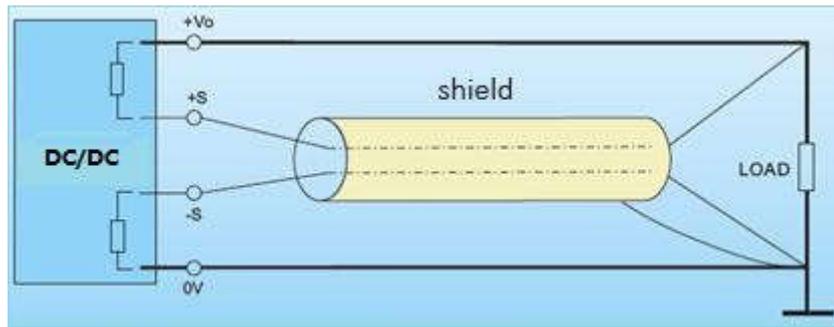


Diagram 3-4 Connection of remote control

DC/DC Converter, in the long-distance transmission, usually uses remote voltage compensation method to improve the input voltage of load, in order to meet the requirement of normal working voltage at full load. The remote voltage compensation method is a method to compensate the input voltage of remote load via pins of + SENSE and -SENSE. When using the wire for remote connection, it should be noted to shield the wire or use twisted pair, as shown in diagram 3-15, in case causing large EMI interference for external wire connection.

c) Switch control

Switch control refers to the converter's output voltage operation of "ON" (enabled) and "OFF" (disabled). There are two standard methods to switch the converter.

Positive logic: CTRL control pin connects with -Vin, output OFF. CTRL control opens or connects high level , output ON.

Negative logic: CTRL control pin connects with -Vin, output ON. CTRL control opens, output OFF.

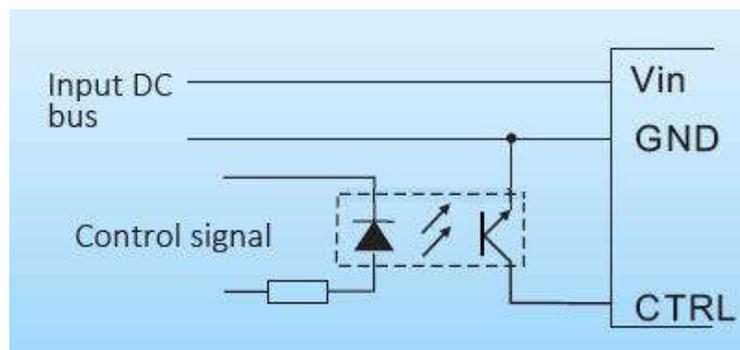


Diagram 3-5 Isolation control method

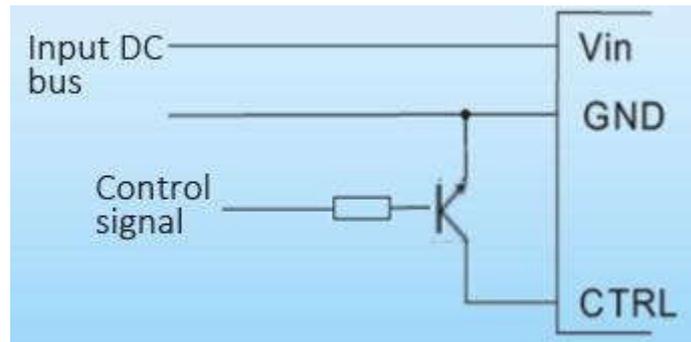


Diagram 3-6 Common control method

In special applications, isolation control method is usually used as shown in diagram 3-16. MORNSUN DC/DC converters are divided into voltage control and current control.

It should change the voltage of the CTRL pin to control the converter's power-on or power-off depending on practical applications and datasheet, when using converters with CTRL pin. If CTRL is not needed, just no connection. If there is some interference in the actual circuit, it is recommended to protect from interference (away from the interference source) in case causing the converter's malfunction or damage.

IV. FAQs

A. Do MORNSUN's DC/DC converters support hot-plug?

"Hot-plug", simply refers to directly unplug or plug converters in the system without power-off.

The converters is not allowed to hot-plug during operation in that it will produce several times or even more of large current and voltage spikes of the converters, affecting internal components and damaging the converters in worse circumstances. Therefore, the converters don't support hot-plug.

B. Can MORNSUN's DC/DC converters be used at no-load or light-load?

The converters can be used at no-load or light-load applications. However, under this condition, the conversion efficiency of the converters is relatively low, oscillation may be produced at no-load, and some indicators may not meet the requirements of datasheet. From the view of reliability, it's better to avoid these applications and the minimum output current of the

converters should be no less than 10% of rated one. It's suggested to use the converters at 30-80% load or choose the converters with lower power.

C. Reasons cause start-up failures of MORNSUN's DC/DC converters?

Reason 1: In actual application, the capacitive load exceeds the maximum value indicated in datasheet. Larger output capacitor requires larger starting current, which will cause the start-up failure of the converters. To reduce the output capacitance at the output terminal or connect buffer circuit is a good choice to increase the capacity of the converters.

Reason 2: Limited to the maximum power provided by the current-sensitive power supply such as intrinsically safe power supply, the starting power cannot meet the requirements of the converters (the converters require a large starting power at start-up). It is recommended to select the products with small starting current or connect a small resistance or NTC at the input terminal of the converters to reduce the start current.

Reason 3: the inductive load (usually motor coil) does not produce induced electromotive force when starting up. Only the coil's resistor r works in the entire loop, will resistance be very small (usually $m\Omega \sim \Omega$ level). According to $I = \frac{V}{r}$, the current will

be larger to exceed the over-current protection value of the converters, triggering the protections of the converters and start-up failures. It is recommended to connect a small resistor in series at the output terminal for converters with low power, or select a power supply with larger power.

D. Operating temperature

When DC/DC Converters work in high temperature environment, their internal components' temperature is much higher than the ambient temperature. In order to ensure the reliability of the converters, the highest environmental operating temperature of conventional converters is 85 °C. When the ambient temperature reached 55 °C or 60 °C, the converters need derating (specific derating curve please refer to datasheet). The lowest ambient temperature for the Mornsun converter is -40°C, and there is no need for derating.

E. Measures to suppress noise

For DC/DC Converters, noise within 20 MHz can be reduced using LC filtering or π filtering, and noise of 100M or 200M should be filtered using a common mode inductor and a capacitor.

F. Over-temperature protection

The power module over 50W generally has over-temperature protection. When choosing the suitable products, customers should confirm the function referring to the datasheet and then consider the appropriate thermal design.

In the actual application, or aging process, there may be no output after working for a period of time. This is because the product has entered the over-temperature protection state. After the temperature drops, the product will restart and the output will be re-established, which is a normal phenomenon. Improving the heat dissipation of the product or derated use can prevent the product entering the over-temperature protection state.

G. Thermal Design Recommendations

The PCB design of the power management circuit plays an important role in the load performance of the power management system under high temperatures. In order to optimize the heat dissipation performance of the power module, it is first necessary to ensure that the

heat of the power module can be quickly transferred to the PCB board and the system shell, and secondly, the heat that transmitted to the PCB board and the system shell must be quickly dissipated;

There are three common heat dissipation methods: convection heat dissipation, radiation heat dissipation, and conduction heat dissipation. Choose the appropriate heat dissipation method according to the actual system.